

Keysight Technologies

Overvoltage Protection in Power Supplies

Application Note



Introduction

Overvoltage (OVP) is an important security feature in power supplies. By using this feature, we can protect the device under test (DUT) from a higher voltage than the DUT was designed to handle. OVP is useful in a variety of applications in electronics manufacturing and the educational market.

Overvoltage protection is also available if required during constant current operation. The constant voltage/constant current (CV/CC) and constant voltage/current limit (CV/CL) automatic crossover circuitry is ideal for these purposes because it allows you to select the maximum safe current or voltage for your particular load device.

Keysight Technologies, Inc. E3600¹ and U8000 series power supplies are short-circuit proof and can operate under any current overload condition indefinitely, without the risk of internal damage. It uses an overvoltage crowbar in which the crowbar circuit is connected across the output terminals. This provides protection against any output overvoltage condition that might occur because of operator error or failure within the power supply or load.

This application note explains the architecture of OVP and describes its applications. It discusses what you need to pay attention to when you use this feature.

Overvoltage Crowbar

An operator error or a component failure in the regulating feedback loop can drive a power supply's output voltage to many times its preset value. The function of the crowbar circuit is to protect the load against this possibility. The circuit ensures that the power supply voltage across the load will never exceed a preset limit. This protection is valuable because of the extreme voltage sensitivity of today's semiconductor devices.

The basic elements used in most crowbars are some method of sensing the output voltage, a silicon controlled rectifier (SCR) that will short the output, and a circuit that will reliably trigger the SCR within a time period that is brief enough to avoid damage to the load.

The sensing circuit can be a simple bridge or voltage divider network that compares the output voltage to the internal crowbar reference voltage. The best trigger circuit is the one that turns on the SCR most quickly. The fastest SCR turn-on is accomplished by a fast rise-time pulse circuit such as a blocking oscillator or Schmitt trigger.

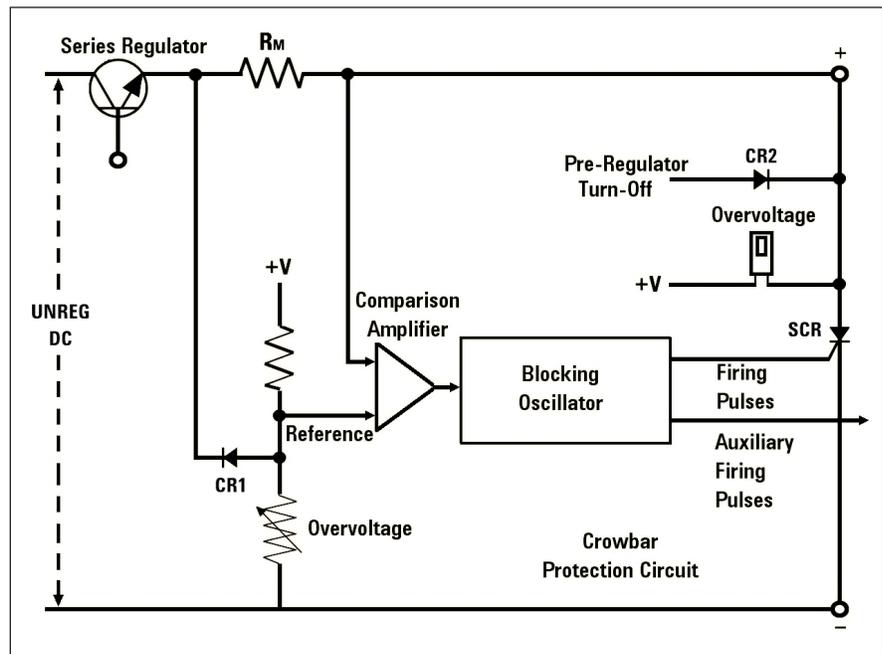


Figure 1. General crowbar overvoltage protection circuit

Figure 1 shows the general crowbar overvoltage protection circuit. The circuit compares the output voltage with a reference voltage +V. The overvoltage potentiometer adjusts the reference voltage on the comparison amplifier and sets the voltage level at which the crowbar will be activated.

Normally, the overvoltage control is located on the front panel and can be adjusted from approximately 20% to 120% of the maximum rated output voltage of the power supply. When the output voltage exceeds the reference, the comparison amplifier triggers the blocking oscillator, which then sends firing pulses to the SCR. When the SCR fires, it places a very low impedance across the output, reducing the voltage to near-zero.

1. Refer to literature 5989-4104EN for the list of power supplies that have OVP

Crowbar circuits have several beneficial features:

- An overvoltage indicator appears when the SCR fires; the indicator conducts a holding current to prevent the SCR from oscillating on and off.
- The crowbar circuit creates an extra current path during normal operation of the supply, thus changing the current that flows through the current monitoring resistor. The diode keeps this extra current at a fixed level where compensation can then be made in the constant-current comparator circuit.
- In pre-regulate supplies, the crowbar turns off the pre-regulator circuit when the SCR fires, reducing the voltage drop across the series regulator and the current flow through the SCR.
- An auxiliary winding is included on the blocking oscillator transformer for connection to an additional crowbar. Tandem crowbar operation is then available for coincident firing of all crowbars in a system.

OVP application

Connect power supply in series

One of the OVP application is to connect power supplies in series for higher voltage output. Set the OVP shutdown voltage in each unit so that it shuts down at a voltage higher than its output voltage during auto-tracking operation. When a master unit shuts down, it programs any slave units to zero output. When a slave unit shuts down, it shuts down only itself, and the master continues to supply output voltage.

Battery charging

Some power supplies contain an overvoltage protection circuit, which will short the power supply's output if an overvoltage condition occurs. The OVP circuit is typically a crowbar SCR that operates independently of the power supply's regulation circuit. When you use a power supply to charge a battery, it is possible to charge the battery to a voltage greater than the OVP limit. Once the OVP limit is exceeded, the SCR will short the output and continuously sink a large current from the source, possibly damaging the power supply. To avoid damaging the power supply, connect a diode in series with the power supply to ensure that current only flows out of the power supply.

False shutdowns

The voltage at the output terminal can be increased inadvertently in a variety of ways such as from the front panel or by a change in the load. False OVP shutdowns can occur if the OVP shutdown voltage has been set too close to the power supply's operating voltage. You should set the OVP shutdown voltage 4% higher or at least +2.0 V above the desired output voltage to avoid false shutdowns from load-induced transients.

False OVP shutdowns occur commonly when the OVP limit is set too close to the output voltage when using remote sensing. Remote sensing will increase the voltage at the output terminals to compensate for the voltage drop in the wire between the power supply and the DUT. A longer cable can create significant voltage drops due to low resistance. Another possible cause of OVP false shutdowns is strong electrostatic discharge (ESD) applied to the power supply, which can trip the OVP limit and eventually crowbar the output, protecting output loads from the hazardous ESD current.

Conclusion

Overvoltage protection is an important feature for power supplies. It can protect your DUT from a voltage higher than it was designed to handle.

By knowing the architecture of a power supply's overvoltage crowbar circuit and its applications, you can easily apply and fully utilize this feature for many applications.

myKeysight

myKeysight

www.keysight.com/find/mykeysight

A personalized view into the information most relevant to you.



www.axiestandard.org

AdvancedTCA® Extensions for Instrumentation and Test (AXIe) is an open standard that extends the AdvancedTCA for general purpose and semiconductor test. Keysight is a founding member of the AXIe consortium. ATCA®, AdvancedTCA®, and the ATCA logo are registered US trademarks of the PCI Industrial Computer Manufacturers Group.



www.lxistandard.org

LAN eXtensions for Instruments puts the power of Ethernet and the Web inside your test systems. Keysight is a founding member of the LXI consortium.



www.pxisa.org

PCI eXtensions for Instrumentation (PXI) modular instrumentation delivers a rugged, PC-based high-performance measurement and automation system.



Three-Year Warranty

www.keysight.com/find/ThreeYearWarranty

Keysight's commitment to superior product quality and lower total cost of ownership. The only test and measurement company with three-year warranty standard on all instruments, worldwide.



Keysight Assurance Plans

www.keysight.com/find/AssurancePlans

Up to five years of protection and no budgetary surprises to ensure your instruments are operating to specification so you can rely on accurate measurements.



www.keysight.com/quality

Keysight Technologies, Inc.
DEKRA Certified ISO 9001:2008
Quality Management System

Keysight Channel Partners

www.keysight.com/find/channelpartners

Get the best of both worlds: Keysight's measurement expertise and product breadth, combined with channel partner convenience.

For more information on Keysight Technologies' products, applications or services, please contact your local Keysight office. The complete list is available at: www.keysight.com/find/contactus

Americas

| | |
|---------------|------------------|
| Canada | (877) 894 4414 |
| Brazil | 55 11 3351 7010 |
| Mexico | 001 800 254 2440 |
| United States | (800) 829 4444 |

Asia Pacific

| | |
|--------------------|----------------|
| Australia | 1 800 629 485 |
| China | 800 810 0189 |
| Hong Kong | 800 938 693 |
| India | 1 800 112 929 |
| Japan | 0120 (421) 345 |
| Korea | 080 769 0800 |
| Malaysia | 1 800 888 848 |
| Singapore | 1 800 375 8100 |
| Taiwan | 0800 047 866 |
| Other AP Countries | (65) 6375 8100 |

Europe & Middle East

| | |
|----------------|---------------|
| Austria | 0800 001122 |
| Belgium | 0800 58580 |
| Finland | 0800 523252 |
| France | 0805 980333 |
| Germany | 0800 6270999 |
| Ireland | 1800 832700 |
| Israel | 1 809 343051 |
| Italy | 800 599100 |
| Luxembourg | +32 800 58580 |
| Netherlands | 0800 0233200 |
| Russia | 8800 5009286 |
| Spain | 0800 000154 |
| Sweden | 0200 882255 |
| Switzerland | 0800 805353 |
| | Opt. 1 (DE) |
| | Opt. 2 (FR) |
| | Opt. 3 (IT) |
| United Kingdom | 0800 0260637 |

For other unlisted countries:
www.keysight.com/find/contactus
(BP-07-10-14)